
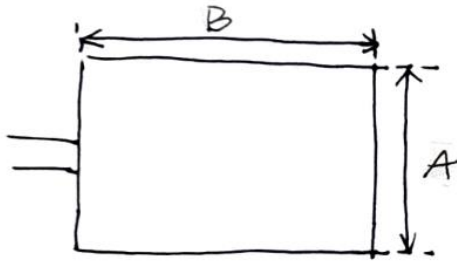


Problem 3.1

1. Resonance frequencies:

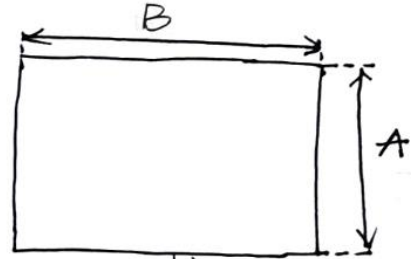

①



②

The function of the resonance frequency can be described as,

$$f_{res} = \frac{c}{\sqrt{\epsilon_{r,eff}} \cdot \lambda_g}$$

$$\text{where } \epsilon_{r,eff} = \frac{\epsilon_r + 1}{2} + \frac{\epsilon_r - 1}{2} \left[1 + 12 \frac{h}{W} \right]^{-\frac{1}{2}}$$

$$\lambda_g = L + 2\Delta L.$$

$$\textcircled{1} \epsilon_{r,eff1} = \frac{\epsilon_r + 1}{2} + \frac{\epsilon_r - 1}{2} \left[1 + 12 \frac{h}{A} \right]^{-\frac{1}{2}} \approx 2.24$$

$$\Delta L = 0.412 h \cdot \frac{\epsilon_{r,eff1} + 0.3}{\epsilon_{r,eff1} - 0.258} \cdot \frac{\frac{A}{h} + 0.262}{\frac{A}{h} + 0.813} \approx 0.0015 \text{ m}$$

$$\lambda_{g1} = B + 2\Delta L = 0.025 \text{ m}$$

$$\text{with } B = 2.2 \text{ cm}, h = 3 \text{ mm}, A = 2 \text{ cm}$$

$$f_{res1} = \frac{c}{\sqrt{\epsilon_{r,eff1}} \cdot \lambda_{g1}} \approx 8.04 \text{ GHz.}$$

$$\textcircled{2} \epsilon_{r,eff2} = \frac{\epsilon_r + 1}{2} + \frac{\epsilon_r - 1}{2} \left[1 + 12 \frac{h}{B} \right]^{-\frac{1}{2}} \approx 2.25$$

$$\Delta L_2 = 0.412 h \cdot \frac{\epsilon_{r,eff2} + 0.3}{\epsilon_{r,eff2} - 0.258} \cdot \frac{\frac{B}{h} + 0.262}{\frac{B}{h} + 0.813} \approx 0.0015 \text{ m}$$

$$\lambda_{g2} = A + 2\Delta L_2 = 0.023 \text{ m}$$

$$\text{with } A = 2 \text{ cm}, h = 3 \text{ mm}, B = 2.2 \text{ cm}$$

$$f_{res2} = \frac{c}{\sqrt{\epsilon_{r,eff2}} \cdot \lambda_{g2}} \approx 8.71 \text{ GHz.}$$

2. Equivalent circuit:

The function of conductance of a single slot is,


$$G_{sl} = \frac{W}{120\lambda_g} \left[1 - \frac{1}{24} \left(2\pi \frac{h}{\lambda_g} \right)^2 \right]$$

The function of characteristic impedance is,


$$Z_0 = \begin{cases} \frac{60}{\sqrt{\epsilon_{r,eff}}} \ln \left(\frac{8h}{W} + \frac{h}{W} \right) & \frac{W}{h} < 1 \\ \frac{120\pi}{\sqrt{\epsilon_{r,eff}} \left(\frac{W}{h} + 1.393 + 0.667 \cdot \ln \left(\frac{W}{h} + 1.444 \right) \right)} & \frac{W}{h} > 1 \end{cases}$$

The results of case ① and case ② are respectively,

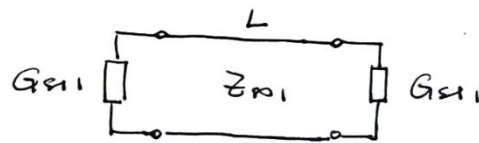
$$G_{sl1} = 0.0065 \text{ S} \quad Z_{01} = 26.65 \Omega$$



$$G_{sl2} = 0.0078 \text{ S} \quad Z_{02} = 24.69 \Omega$$

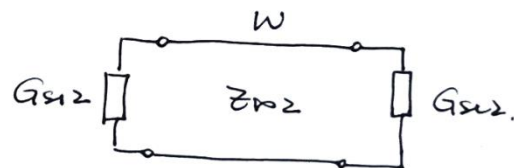

Problem 3.2

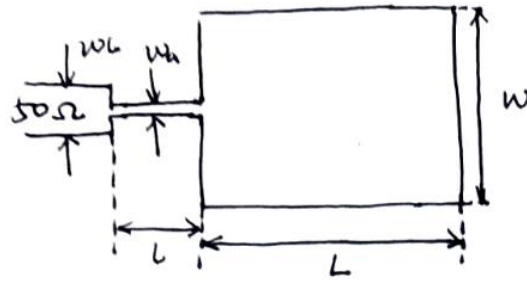

The optimum width of the microstrip radiator is,

$$W_{opt} = \frac{c}{2f\sqrt{\epsilon_r}} \sqrt{\frac{2}{\epsilon_r + 1}} = \frac{3 \times 10^8}{2 \times 2.54 \times 10^9} \sqrt{\frac{2}{2.56 + 1}} \approx 0.044 \text{ m}$$

The patch length can be calculated with,

$$L + \Delta L = \frac{\lambda_g}{2}$$

where ΔL is the extension length, and $\lambda_g = \frac{\lambda_0}{\sqrt{\epsilon_{r,eff}}}$.

ΔL can be obtained by, $(\lambda_0 = \frac{c}{f} \approx 0.12 \text{ m})$

$$\frac{\Delta L}{h} = 0.412 \frac{\epsilon_{r,eff} + 0.3}{\epsilon_{r,eff} - 0.258} \cdot \frac{\frac{w}{h} + 0.262}{\frac{w}{h} + 0.813}$$


$$\text{with } \epsilon_{r,eff} = \frac{\epsilon_r + 1}{2} + \frac{\epsilon_r - 1}{2} \left[1 + 12 \frac{h}{w} \right]^{-\frac{1}{2}} \approx 2.43$$

Therefore $\Delta L = 8.06 \times 10^{-4} \text{ m}$, $\lambda_g = 0.076 \text{ m}$

$$L = \frac{\lambda_g}{2} - \Delta L = 0.037 \text{ m}$$

The conductance of the patch can be equivalently obtained as,

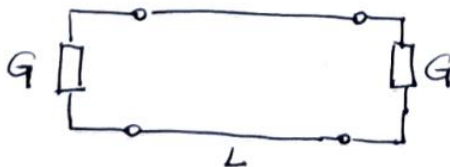
$$G = \frac{w}{120\lambda_0} \left[1 - \frac{1}{24} \left(2\pi \frac{h}{\lambda_0} \right)^2 \right] \approx 0.0031 \text{ S}$$



The equivalent impedance of the patch is then,

$$Z_p = \frac{1}{2G} \approx 160.15 \Omega$$

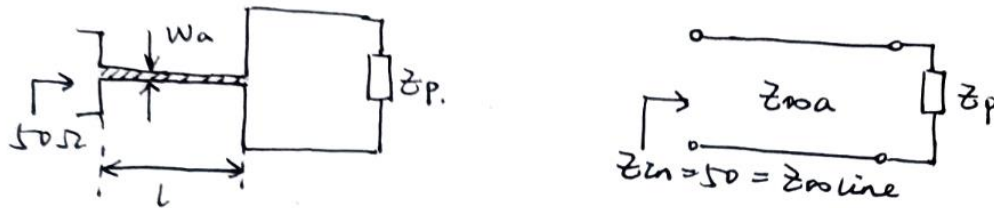The equivalent circuit of the middle section of the substrate can be shown as,



$$Z_{0a} = \sqrt{Z_{0line} \cdot Z_p} \approx 89.48 \Omega$$

due to the transmission line theory, as with $\frac{\lambda}{4}$ matching.

With $Z_{0line} = 50\Omega$, $Z_{0a} = 89.48\Omega$

the width W_b and W_a can be obtained using the functions,

$$\frac{W}{h} = \begin{cases} \frac{8e^A}{e^{2A} - 2} & \frac{W}{h} < 2 \\ \frac{2}{\pi} \left\{ B - 1 - \ln(2B - 1) + \frac{\epsilon_r - 1}{2\epsilon_r} C \right\} & \frac{W}{h} > 2 \end{cases}$$

where $A = \frac{Z_0}{60} \sqrt{\frac{\epsilon_r + 1}{2}} + \frac{\epsilon_r - 1}{\epsilon_r + 1} \left(0.23 + \frac{0.11}{\epsilon_r} \right)$

$$B = \frac{377\pi}{2Z_0\sqrt{\epsilon_r}}$$


$$C = \ln(2B - 1) + 0.39 - \frac{0.61}{\epsilon_r}$$

Finally, $W_b = 0.0044 = 4.4 \text{ mm}$

$$W_a = 0.0016 = 1.6 \text{ mm}$$



$$L_a = \frac{\lambda_g}{4} = 18.9 \text{ mm.}$$

Problem 3.3

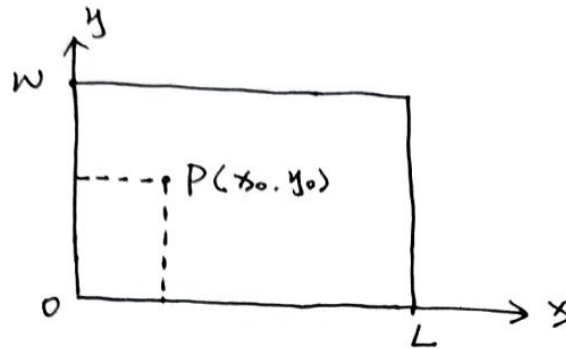

Assuming the rectangular patch antenna is positioned in the coordinate system as above, with the feeding point at a random position of (x_0, y_0) .

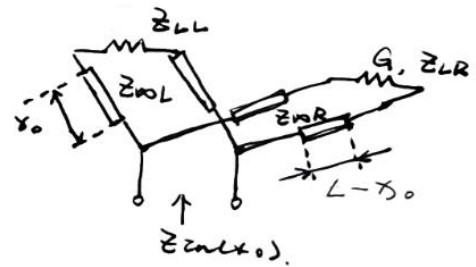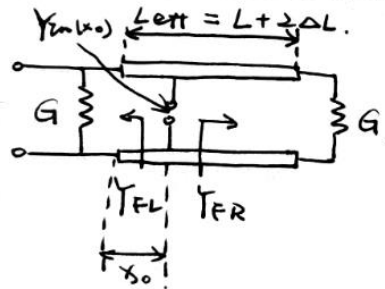The equivalent transmission line model can be shown as.



$$Y_{in}(x_0) = Y_{FL}(x_0) + Y_{FR}(x_0).$$

$$\text{and } G = \frac{W}{120\lambda_0} \left[1 - \frac{1}{24} \left(2\pi \frac{h}{\lambda_0} \right)^2 \right] = \frac{1}{Z_{LR}} = \frac{1}{Z_{LL}}$$

$$Y_{FR} = \frac{1}{Z_{0R}} \frac{Z_{0R} + j Z_{LR} \tan[k(L - x_0)]}{Z_{LR} + j Z_{0R} \tan[k(L - x_0)]}$$

$$Y_{FL} = \frac{1}{Z_{0L}} \frac{Z_{0L} + j Z_{LL} \tan(k x_0)}{Z_{LL} + j Z_{0L} \tan(k x_0)}$$

$Z_{0R} = Z_{0L}$, as Z_{00} is only related to W , h and ϵ_r , with

$$Z_{00} = \begin{cases} \frac{60}{\sqrt{\epsilon_{r,eff}}} \left(\ln \frac{8h}{W} + \frac{h}{W} \right) & \frac{W}{h} < 1 \\ \frac{120\pi}{\sqrt{\epsilon_{r,eff}}} \left[\frac{W}{h} + 1.393 + 0.667 \cdot \ln \frac{W}{h} + 1.444 \right] & \frac{W}{h} > 1 \end{cases}$$

$$\text{where } \epsilon_{r,eff} = \frac{\epsilon_r + 1}{2} - \frac{\epsilon_r - 1}{2} \left(1 + 12 \frac{h}{W} \right)^{-\frac{1}{2}}$$

Also, $Z_{LL} = Z_{LR} = \frac{1}{G}$

Therefore, the only difference of Y_{FR} and Y_{FL} is related on $\tan(kx_0)$ and $\tan[k(L-x_0)]$, where,

$$\tan[k(L-x_0)] = \frac{\tan kL - \tan kx_0}{1 + \tan kL \cdot \tan kx_0}$$

Then, Assume $Z_{DL} = Z_{DR} = Z_m$, $Z_{LL} = Z_{LR} = Z_L$.

Let $\tan kL = A$, $\tan kx_0 = B$

The combination function of $Y_{in}(x_0) = Y_{FR} + Y_{FL}$ could be simplified as,

$$Y_{in} = \frac{1}{Z_m} \frac{2Z_m Z_L (1 - B^2) + j(Z_m^2 + Z_L^2) A (1 + B^2)}{Z_L^2 (1 + AB) - Z_m^2 B(A - B) + jZ_L Z_m A (1 + B^2)}$$